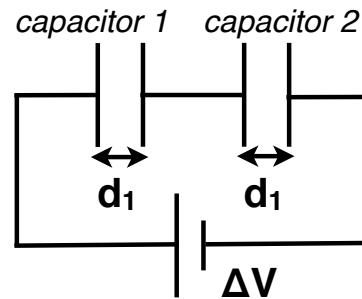



7. Capacitor Networks – II.

Two air-filled capacitors of plate area A and plate separation d_1 are connected to a battery, as depicted to the right. For the purposes of this question, take the permittivity of air to be equal to ϵ_0 , the permittivity of free space.



a) Derive the equivalent capacitance of the circuit depicted in the upper diagram using A , d_1 and ϵ_0

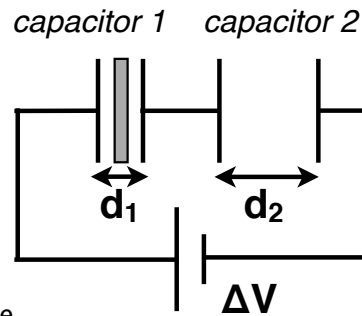b) Pokium has a dielectric constant of K_p . A slab of pokium with a thickness of $d_1/3$ and an area A (the same area as the capacitor plates) is placed in capacitor 1, as depicted to the right. Capacitor 1 now has a series of $d_1/3$ of air, then $d_1/3$ of pokium, then $d_1/3$ of air between its plates. Find the equivalent capacitance of this new circuit using A , d_1 , K_p , ϵ_0 and d_2 , where d_2 is the plate separation for capacitor 2.



c) $K_p = 2.0$ is the dielectric constant of pokium. If the two depicted circuits were set up to have the same equivalent capacitance, and $d_1 = 3.0\text{cm}$, what would be the value of d_2 , the plate separation for capacitor 2, in cm?

d) $\epsilon_0 = 8.9 \times 10^{-12} \text{ F/m}$, $A = 10.0 \text{ cm}^2$, and the battery supplies $\Delta V = 12 \text{ V}$. In the final configuration of the circuit depicted in the lower diagram, for d_2 as calculated in part (c) of this problem, what is the stored energy in capacitor 2?

Hint: note that the equivalent capacitance was set up to be the same for the two depicted circuits.

(a)(i) WHAT IS THE EXPRESSION FOR CAPACITANCE BASED ON THE PHYSICAL CHARACTERISTICS OF A CAPACITOR? (ii) WHAT IS THE EXPRESSION FOR EQUIVALENT CAPACITANCE FOR MULTIPLE CAPACITORS IN SERIES (C_{EQ})?

(b) (i) ARE THE COMPONENTS OF CAPACITOR 1 IN SERIES OR IN PARALLEL? (ii) SO, WHAT IS AN EXPRESSION FOR C_1 BASED ON SUMMING ITS COMPONENTS IN SERIES OR PARALLEL? (iii) WHAT IS AN EXPRESSION FOR C_2 (AS FOR PART (a))? (iv) SO, WHAT IS AN EXPRESSION FOR C_{EQ} FOR THE SECOND CIRCUIT?

(c) TO FIND WHEN THE CIRCUITS HAVE THE SAME C_{EQ} , EQUATE YOUR EQUATIONS FROM (a) AND (b). NOTE THAT IF $C_{EQ} = C'_{EQ}$ THEN $\frac{1}{C_{EQ}} = \frac{1}{C'_{EQ}}$ SO LEAVING YOUR EXPRESSIONS AS $\frac{1}{C_{EQ}} =$ MAY BE QUICKER

(d)(i) IN SERIES, IS THE CHARGE THE SAME ACROSS ALL ELEMENTS, OR IS IT THE VOLTAGE? (ii) FOR THE STORED ENERGY IN CAPACITOR 2 YOU WILL NEED TO FIND $U_2 = \frac{1}{2} C_2 V_2^2$ BUT V_2 MAY NOT EQUAL V ACROSS THE ENTIRE CIRCUIT (iii) FIND C_2 IN TERMS OF ITS PHYSICAL CHARACTERISTICS (LIKE IN PART (a)) (iv) USE C_{EQ} (ALSO CALCULATED IN PART (a))... SEE THE QUESTION HINT) TO FIND V_2 IF $C_2 = \frac{Q_2}{V_2}$ AND $C_{EQ} = \frac{Q}{V}$ (v) HENCE FIND U_2
