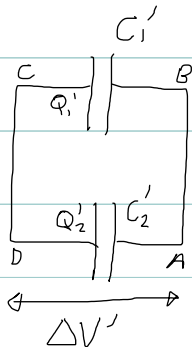


(B) FINAL CONFIGURATION



TWO CAPACITORS OF CAPACITANCE  $C_1$  AND  $C_2$  ARE CHARGED BY A POTENTIAL DIFFERENCE OF VOLTAGE  $\Delta V$  AND HENCE ACQUIRE CHARGE OF  $Q_1$  AND  $Q_2$ . THE

BATTERY THAT CHARGED THE CAPACITORS IS THEN


REMOVED. THE CAPACITORS ARE THEN CONNECTED

TO EACH OTHER AS IN DIAGRAM (B). WHAT IS THE

VOLTAGE BETWEEN POINTS B AND C IN DIAGRAM (B)?

HENCE, WHAT IS THE NEW CHARGE ON EACH

CAPACITOR  $Q_1'$  AND  $Q_2'$ ?

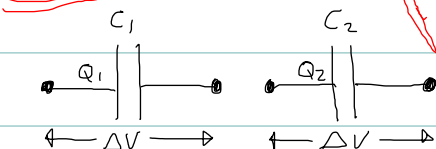

(A) CHARGING CONFIGURATION

(1) THE VOLTAGE BETWEEN B AND C. THE RE-CONNECTED CAPACITORS ARE IN PARALLEL BECAUSE THEY HAD THE SAME POTENTIAL DIFFERENCE ACROSS THEM. THE FOLLOWING RULES

APPLY: (a) THE TOTAL CHARGE FROM SITUATION (A) TO SITUATION (B) IS CONSERVED  $\Rightarrow$

$Q_1 + Q_2 = Q_1' + Q_2'$  (b) THE CAPACITORS ARE PHYSICALLY UNCHANGED  $\Rightarrow C_1 = C_1'$  and  $C_2 = C_2'$

(c) THE POTENTIAL ACROSS EACH CAPACITOR IS THE SAME IN PARALLEL  $\Rightarrow \Delta V' = \Delta V_1' = \Delta V_2'$

NOW,  $V_B - V_C = V_A - V_D = \Delta V' = \frac{Q_{TOT}'}{C_{EQ}'}$ . IN PARALLEL  $C_{EQ}' = C_1' + C_2'$ , WHICH IS  $C_1 + C_2$ , HERE

ALSO,  $Q_{TOT}' = Q_1' + Q_2'$ , WHICH IS  $Q_1 + Q_2$ , HERE.

$$\Rightarrow V_B - V_C = \frac{Q_{TOT}'}{C_{EQ}'} = \frac{Q_1' + Q_2'}{C_1' + C_2'} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

(2) THE NEW CHARGE ON EACH CAPACITOR,  $Q_1'$  AND  $Q_2'$

WE KNOW FROM THE ANSWER TO PART (1) THAT  $V_B - V_C = V_A - V_D = \frac{Q_1 + Q_2}{C_1 + C_2}$

THE CHARGE ACROSS CAPACITOR 1 IS  $Q_1' = C_1' \Delta V'$ , WHICH IS  $C_1' (V_B - V_C) = C_1' \left( \frac{Q_1 + Q_2}{C_1 + C_2} \right)$

AS  $C_1' = C_1$ ,  $Q_1' = C_1 \left( \frac{Q_1 + Q_2}{C_1 + C_2} \right)$ , SIMILARLY,  $Q_2' = C_2 \left( \frac{Q_1 + Q_2}{C_1 + C_2} \right)$